

EEL 3712L LOGIC DESIGN I LAB

Practice for Final – Summer, 2019

Instructor: Abdullah Aydeger

1. Design a *half* adder/subtract Circuit with XOR, AND and Inverter (whichever needed) gates.

Answer:

Symbol	Truth Table			
	B	A	SUM	CARRY
	0	0	0	0
	0	1	1	0
	1	0	1	0
	1	1	0	1


$$\text{SUM} = A \text{ XOR } B = A \oplus B$$

$$\text{CARRY} = A \text{ AND } B = A \cdot B$$

Half Subtractor with Borrow-out

$$D = X \text{ XOR } Y = X \oplus Y$$


$$B = \text{not-}X \text{ AND } Y$$

 

Symbol	Truth Table			
	Y	X	DIFFERENCE	BORROW
	0	0	0	0
	0	1	1	0
	1	0	1	1
	1	1	0	0

2. Design a 4-to-1 Multiplexer with gates and invertors.
 - a. Make the Truth table and the equation, you may use De Morgan' Law convert into universal gates(NAND and NOR) for the diagram
 - b. Draw the diagram
 - c. Complete the waveform
 - d. Design Half-adder using this MUX(es).


2² X 1 Multiplexer Waveform

 



Answer: $Y = S_1' \cdot S_0' \cdot X_0 + S_1' \cdot S_0 \cdot X_1 + S_1 \cdot S_0' \cdot X_2 + S_1 \cdot S_0 \cdot X_3$

4 X 1 Multiplexer Truth Table

Inputs						Output
S ₀	S ₁	X ₀	X ₁	X ₂	X ₃	Y
0	0	0	x	x	x	0
0	0	1	x	x	x	1
1	0	x	0	x	x	0
1	0	x	1	x	x	1
0	1	x	x	0	x	0
0	1	x	x	1	x	1
1	1	x	x	x	0	0
1	1	x	x	x	1	1

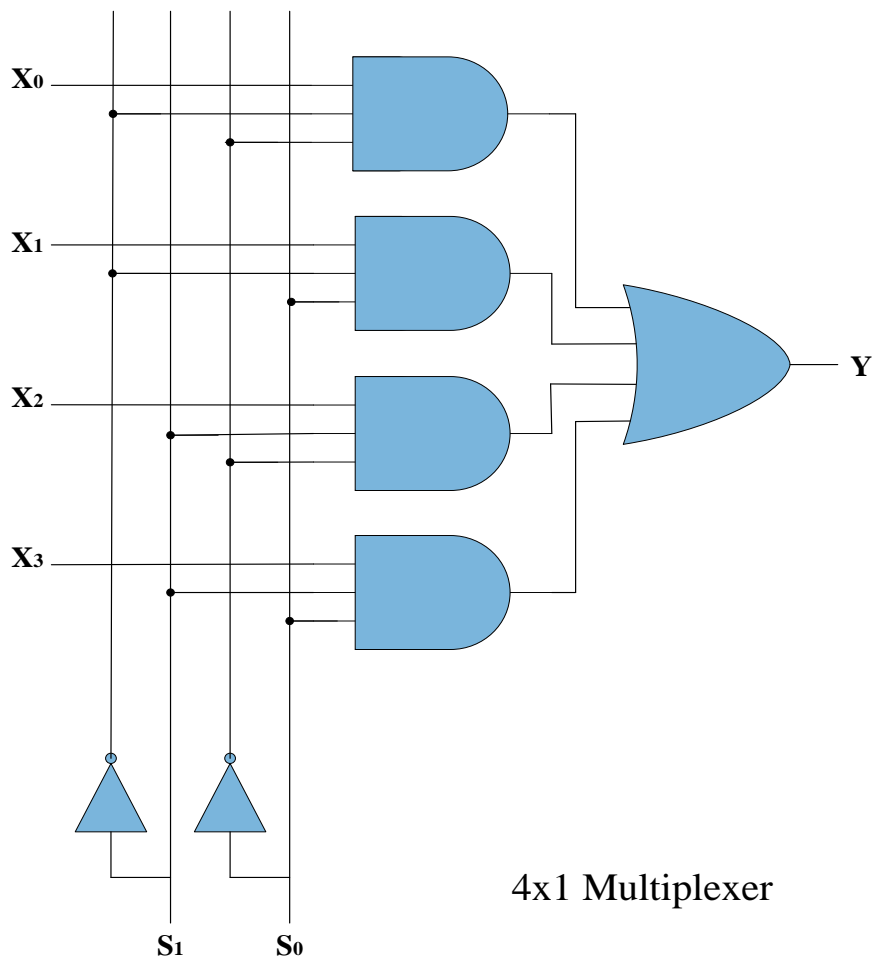

2² x 1 Multiplexer Wave Form

  


S = sum

C = carry-out

A and B are inputs (A+B)

 3. 7-Segment Octal Number (from 0 to 7) display driver could display the octal number given by the three inputs I₂I₁I₀ using a 7-Segment LED device as shown in Fig 1. The truth table for this circuit is in Tab. 4, please fill in it and write the Minterms of each segment of LED display for this driver.



Binary-coded Octal to 7-Segment Display Decoder Truth Table

Decoder Input			Decoder Outputs (Octal#)	Inputs of Common Cathode 7-Segment LED Display						
I ₂	I ₁	I ₀		a	b	c	d	e	f	g

Write Minterms of:

a = $\Sigma (0, 2, 3, 5, 6, 7)$

b =

e =

c =

f =

d =

g =

Answer:

Binary-coded Octal to 7-Segment Display Decoder Truth Table

Decoder Input			Decoder Outputs (Octal#)	Inputs of Common Cathode 7-Segment LED Display						
I ₂	I ₁	I ₀		a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	1	1	0	1	1	0	0	0	0
0	1	0	2	1	1	0	1	1	0	1
0	1	1	3	1	1	1	1	0	0	1
1	0	0	4	0	1	1	0	0	1	1
1	0	1	5	1	0	1	1	0	1	1
1	1	0	6	1	0	1	1	1	1	1
1	1	1	7	1	1	1	0	0	0	0

$$a = \sum (0, 2, 3, 5, 6, 7)$$

$$e = \sum (0, 2, 6)$$

$$b = \sum (0, 1, 2, 3, 4, 7)$$

$$f = \sum (0, 4, 5, 6)$$


$$c = \sum (0, 1, 3, 4, 5, 6, 7)$$

$$g = \sum (2, 3, 4, 5, 6)$$


$$d = \sum (0, 2, 3, 5, 6)$$

4. Design **Active-High** Output 2 to 4 Binary Decoder using AND gates. Consider Enable input for your design. Show the truth table. By using this decoder, design 3 to 8 decoder.


Answer:

 

Enable	Inputs		Outputs			
E	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

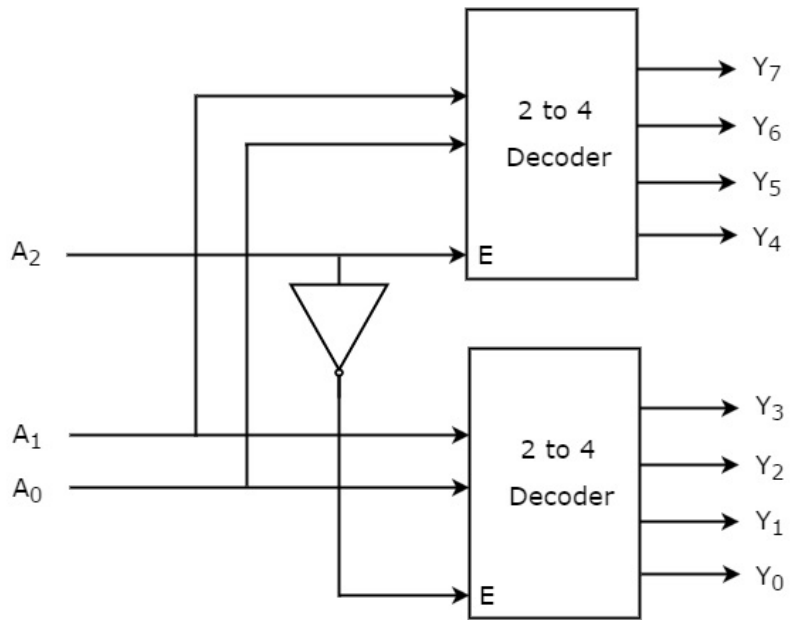

 5. (a) Construct truth table of the schematic.
 (b) Write the expression (equation) of $Z = f(a,b,c,d)$.
 (c) Design and draw same function using 4:16 decoder.



Answer:


Truth table:

a	b	c	d	z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

$$z = a'b'cd' + a'b'cd + a'bc'd' + a'bcd' + ab'c'd' + ab'cd + abc'd' + abc'd$$

Remember that $a'b'c'd' + a'b'c'd = a'b'c'(d' + d) = a'b'c'$


c.

 

6. Write the truth table of following function and then design the schematic using MUX(es) and 2 inverter gates.

If $s_0 = 0$ then $z = f(a,b,c) = a'b + bc + b'c'$

If $s_0 = 1$ then $z = \bar{f}(a,b,c)$

 

Answer:

a	b	c	f(S=0)	
0	0	0	1	c'
0	0	1	0	
0	1	0	1	1
0	1	1	1	
1	0	0	1	c'
1	0	1	0	
1	1	0	0	c
1	1	1	1	

