



# EXPERIMENT 9

## Multiplexers & De-Multiplexers

*Department of Electrical & Computer Engineering*

### I. OBJECTIVES:

- Examine the functions of multiplexers (MUX) and demultiplexers (DEMUX).
- Create an 8-to-1 MUX in schematic mode and simulate the design.
- Create a 1-of-8 DEMUX in schematic mode and test the design on a target board.
- Compare the characteristics of the 1-of-8 DEMUX with the 3-to-8 decoder.

### II. MATERIALS:

- Xilinx Vivado software, student or professional edition V2018.2 or higher.
- IBM or compatible computer with Pentium III or higher, 128 M-byte RAM or more, and 8 G-byte Or larger hard drive.
- BASYS 3 Board.

### III. DISCUSSION:

A multiplexer (MUX) is a logic circuit that channels two or more input data lines to one output data line. A MUX is also called a data selector. The routing of a particular data input to the output is controlled by the SELECT (or ADDRESS) inputs. Generally speaking, a MUX has  $N$  select inputs (address bits),  $2N$  data inputs, and one data output. For example, an 8-to-1 MUX has eight data inputs, three select inputs, and one output.


Multiplexers are widely used in digital and data communication systems. They can perform data selection, data routing, operation sequencing, parallel-to-serial conversion, waveform generation, and logic-function generation. Multiplexers make it possible for several streams of digital data to be sent over one physical cable in a system called TDM (time-division-multiplexing) or TDMA (time-division-multiple-access).

A demultiplexer (DEMUX) performs the reverse operation of a MUX. A DEMUX is also called a data distributor. It selects a single data stream (channel) out of the several coming in and routes it to the appropriate output. The channel is chosen by putting its binary address on the select (address) inputs. A DEMUX has one data input,  $N$  select inputs, and  $2^N$  output lines. For instance, a 1-of-16 DEMUX has one data input, four select inputs, and 16 outputs.

## 1. The 8-to-1 MUX (74151)

The 8-to-1 MUX accepts one of the eight data inputs and passes the data to the output depending on the status of the select lines. Table 10.1 describes the function of this MUX.

Figure 9.1 Diagram of 74151

 

TRUTH TABLE

$\bar{E}$	$S_2$	$S_1$	$S_0$	$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$	$\bar{Z}$	Z
H	X	X	X	X	X	X	X	X	X	X	X	H	L
L	L	L	L	L	X	X	X	X	X	X	X	H	L
L	L	L	L	H	X	X	X	X	X	X	X	L	H
L	L	L	H	X	L	X	X	X	X	X	X	H	L
L	L	L	H	X	H	X	X	X	X	X	X	L	H
L	L	H	L	X	X	L	X	X	X	X	X	H	L
L	L	H	L	X	X	H	X	X	X	X	X	L	H
L	L	H	H	X	X	X	L	X	X	X	X	H	L
L	L	H	H	X	X	X	H	X	X	X	X	L	H
L	H	L	L	X	X	X	X	L	X	X	X	H	L
L	H	L	L	X	X	X	X	H	X	X	X	L	H
L	H	L	H	X	X	X	X	X	L	X	X	H	L
L	H	L	H	X	X	X	X	X	H	X	X	L	H
L	H	H	L	X	X	X	X	X	X	L	X	H	L
L	H	H	L	X	X	X	X	X	X	H	X	L	H
L	H	H	H	X	X	X	X	X	X	X	L	H	L
L	H	H	H	X	X	X	X	X	X	X	H	L	H

H = HIGH Voltage Level  
 L = LOW Voltage Level  
 X = Don't Care


Table 9.2 Truth Table for the 8-to-1 MUX (74151)

In the truth table, E is the gate (enable) input and A, B, and C are select inputs; **I<sub>0</sub>** through **I<sub>7</sub>** are data inputs. Since the enable input is active-low, an input channel can be selected only when the enable line is LOW. An input channel is selected by placing its binary address on the inputs A, B, and C. For example, when **ABC=110**, the output on **Y** will be the **D<sub>6</sub>** bit stream.

## 2. The 1-of-8 DEMUX

In CPLD Experiment 8, we examined decoders. Given a 3-to-8 decoder with an enable input, we had three data inputs, one enable input, and eight outputs. However, the same circuit can be used for a different function. Specifically, we can use the enable input as a data input, and the three data inputs as select inputs. The result is that the 3-to-8 decoder becomes a 1-of-8 demultiplexer, as illustrated in Figure 10.1 below.


Figure 9.3

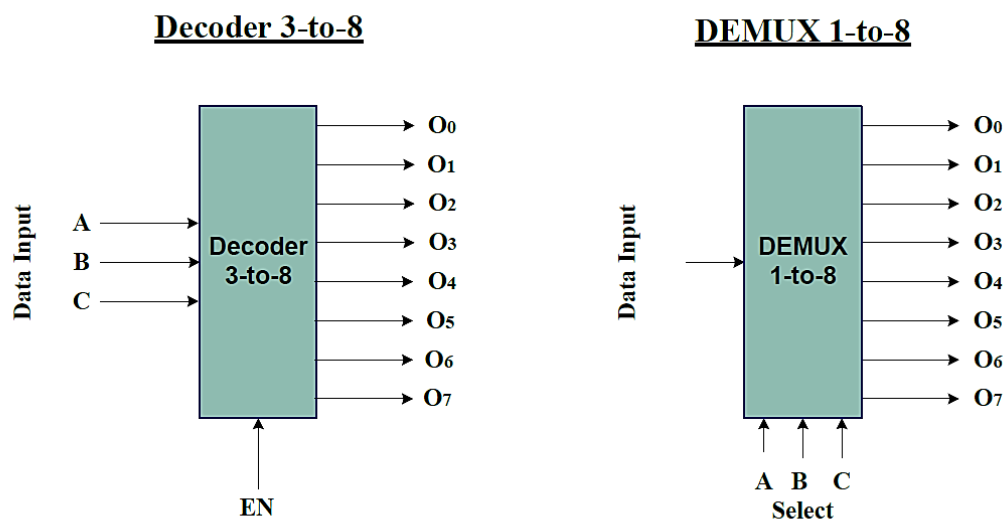

## IV. **PROCEDURE:** Section I. The 8-to-1 MUX

1. Open Xilinx Vivado and in the **Xilinx-Project Navigator** window, Quick start, **New Project**.

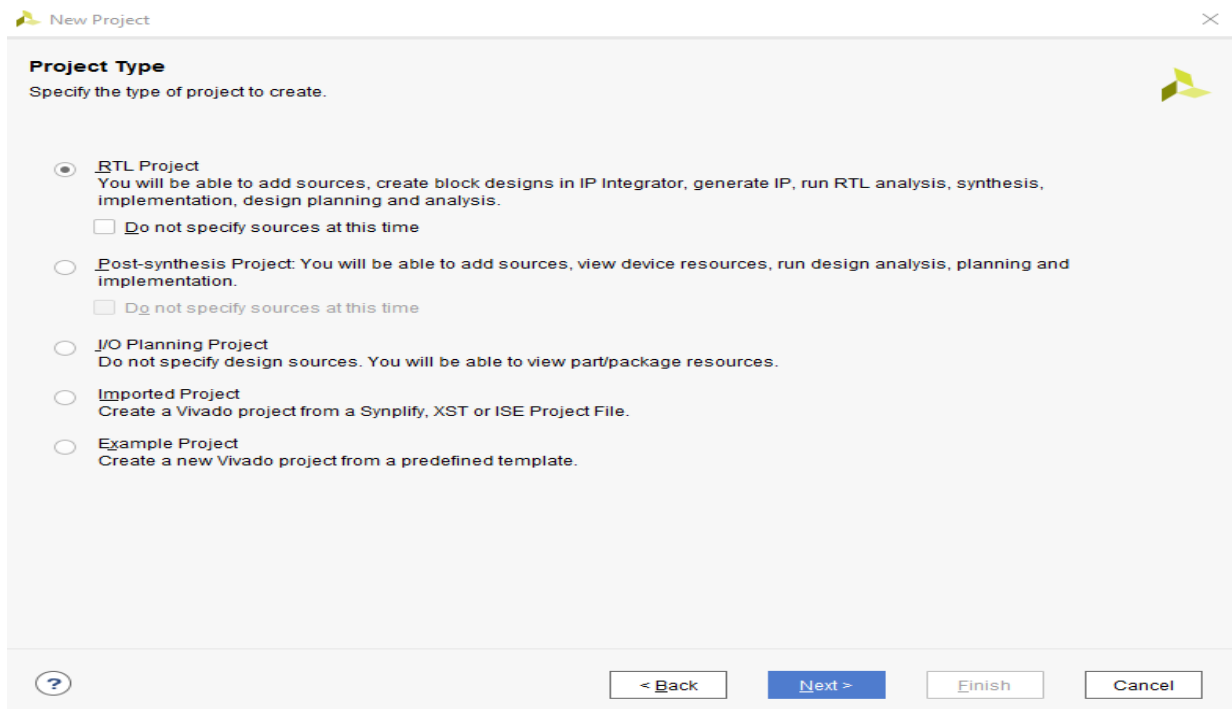2. Choose “RTL Project” and check the “Do not specify sources at this time” as we will configure all the settings manually through the navigator from inside the project.



3. Select **New Source...** and the **New** window appears. In the **New** window, choose Schematic, type your file name (such as **MUX**) in the File Name editor box, click on OK, and then click on the Next button.

4. In the **Xilinx - Project Navigator** window, select the following
  - Category: “General Purpose”
  - Family: “Artix-7”
  - Package: “cpg236”
  - Speed: “-1”
  - Choose “xc7a35tcpg236-1” that corresponds to the board we are using.
  - Then choose Finish.

- The Define Module Window that will appear, we will choose the input and output labels for the gates under investigation in this experiment as shown below.

Define a module and specify I/O Ports to add to your source file.  
For each port specified:  
MSB and LSB values will be ignored unless its Bus column is checked.  
Ports with blank names will not be written.

**Module Definition**

Entity name: MUX

Architecture name: Behavioral

**I/O Port Definitions**

Port Name	Direction	Bus	MSB	LSB
D	in	<input checked="" type="checkbox"/>	7	0
S	in	<input checked="" type="checkbox"/>	2	0
Y	out	<input type="checkbox"/>	0	0

OK Cancel

- In the “MUX.vhd” created file, type the gates equivalent VHDL code for the 8 X 1 MUX between the “begin” and “end Behavioral” as follows and then save the file.

```

28
29  -- Uncomment the following library declaration if instantiating
30  -- any Xilinx leaf cells in this code.
31  --library UNISIM;
32  --use UNISIM.VComponents.all;
33
34  entity MUX is
35      Port ( S : in STD_LOGIC_VECTOR (2 downto 0);
36            D : in STD_LOGIC_VECTOR (7 downto 0);
37            Y : out STD_LOGIC);
38  end MUX;
39
40  architecture Behavioral of MUX is
41
42  begin
43
44  with S select
45      Y <= D(0) when "000",
46           D(1) when "001",
47           D(2) when "010",
48           D(3) when "011",
49           D(4) when "100",
50           D(5) when "101",
51           D(6) when "110",
52           D(7) when "111",
53           '0' when others;
54  end Behavioral;
55

```




7. Next, we need to add To add a constraint file with the ".xdc" extension, as following:


```
11 ## Switches
12 set_property PACKAGE_PIN V17 [get_ports {D[0]}]
13     set_property IOSTANDARD LVCMOS33 [get_ports {D[0]}]
14 set_property PACKAGE_PIN V16 [get_ports {D[1]}]
15     set_property IOSTANDARD LVCMOS33 [get_ports {D[1]}]
16 set_property PACKAGE_PIN W16 [get_ports {D[2]}]
17     set_property IOSTANDARD LVCMOS33 [get_ports {D[2]}]
18 set_property PACKAGE_PIN W17 [get_ports {D[3]}]
19     set_property IOSTANDARD LVCMOS33 [get_ports {D[3]}]
20 set_property PACKAGE_PIN W15 [get_ports {D[4]}]
21     set_property IOSTANDARD LVCMOS33 [get_ports {D[4]}]
22 set_property PACKAGE_PIN V15 [get_ports {D[5]}]
23     set_property IOSTANDARD LVCMOS33 [get_ports {D[5]}]
24 set_property PACKAGE_PIN W14 [get_ports {D[6]}]
25     set_property IOSTANDARD LVCMOS33 [get_ports {D[6]}]
26 set_property PACKAGE_PIN W13 [get_ports {D[7]}]
27     set_property IOSTANDARD LVCMOS33 [get_ports {D[7]}]
28 set_property PACKAGE_PIN V2 [get_ports {S[0]}]
29     set_property IOSTANDARD LVCMOS33 [get_ports {S[0]}]
30 set_property PACKAGE_PIN T3 [get_ports {S[1]}]
31     set_property IOSTANDARD LVCMOS33 [get_ports {S[1]}]
32 set_property PACKAGE_PIN T2 [get_ports {S[2]}]
33     set_property IOSTANDARD LVCMOS33 [get_ports {S[2]}]

46 ## LEDs
47 set_property PACKAGE_PIN U16 [get_ports {Y}]
48     set_property IOSTANDARD LVCMOS33 [get_ports {Y}]
```

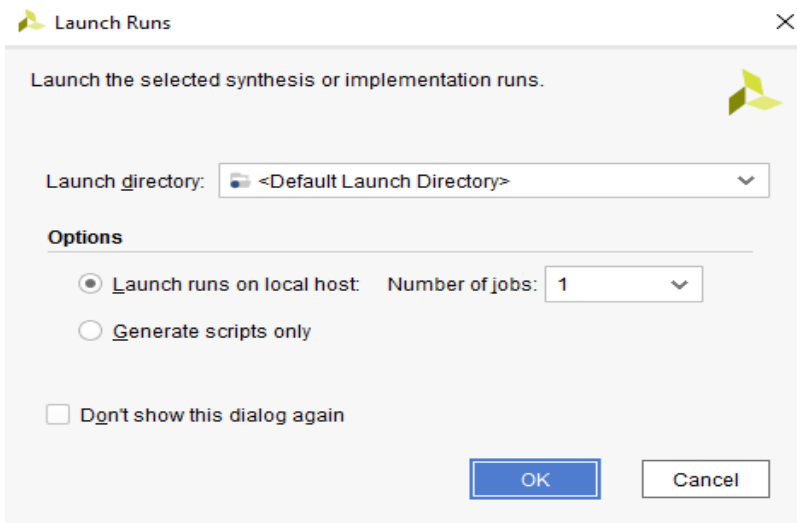
8. From the tool tab choose the play button  and then "Run Implementation". Select "Number of jobs" =1 and then press OK.



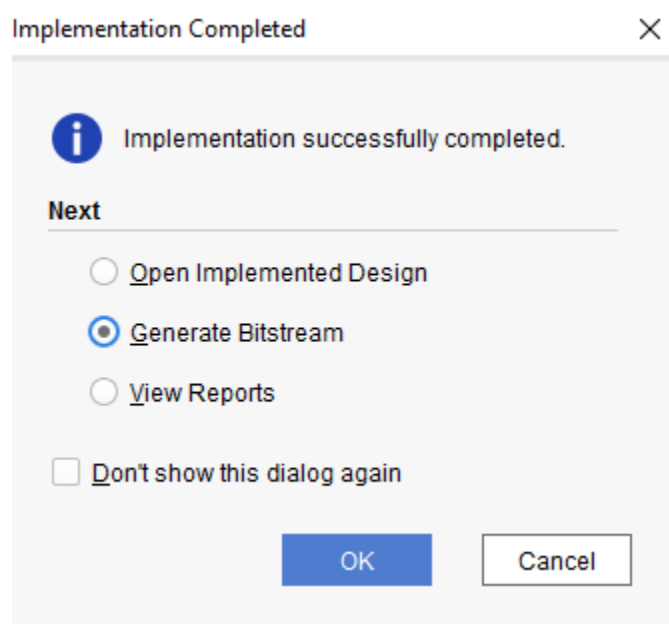9. The implementation errors window will appear if any or the successfully completed window. From this window select “Generate Bitstream” and then OK. This will make the software generate “.bin” file to be used in programming the hardware BAYAS 3.



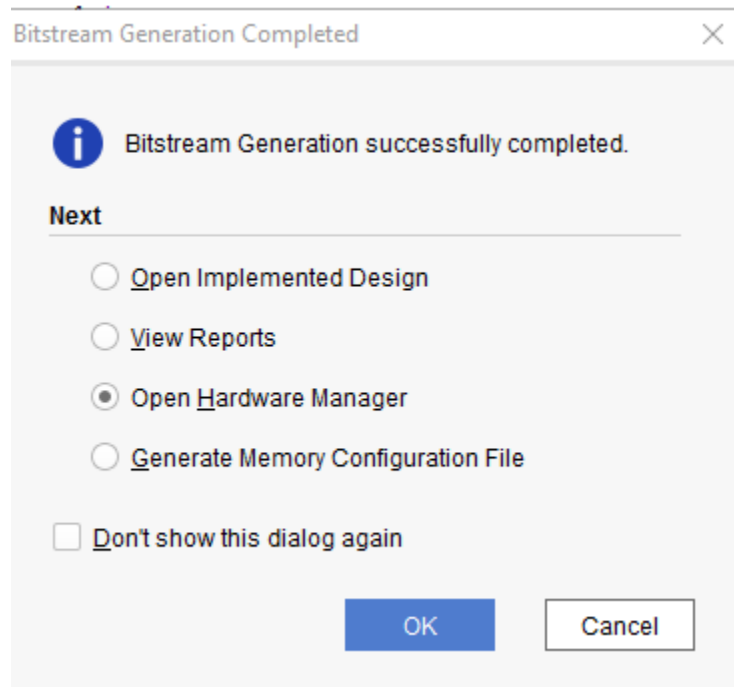10. The next window will appear in which choose “Open Hardware Manger”, connect the Hardware Kit to the USB port and then press OK.







## Section II. The 1-to-8 DEMUX

1. Repeat steps from 1 to 5 in section I
2. The Define Module Window that will appear, we will choose the input and output labels for the gates under investigation in this experiment as shown below.

Define a module and specify I/O Ports to add to your source file.  
For each port specified:  
MSB and LSB values will be ignored unless its Bus column is checked.  
Ports with blank names will not be written.

**Module Definition**

Entity name: DEMUX

Architecture name: Behavioral

**I/O Port Definitions**

Port Name	Direction	Bus	MSB	LSB
Y	in	<input type="checkbox"/>	0	0
A	in	<input checked="" type="checkbox"/>	2	0
D	out	<input checked="" type="checkbox"/>	7	0

OK Cancel

3. In the “DEMUX.vhd” created file, type the gates equivalent VHDL code for the 1-to-8 DEMUX between the “begin” and “end Behavioral” as follows and then save the file.

```

31 | --library UNISIM;
32 | --use UNISIM.VComponents.all;
33 |
34 | entity DEMUX is
35 |     Port ( Y : in STD_LOGIC;
36 |           A : in STD_LOGIC_VECTOR (2 downto 0);
37 |           D : out STD_LOGIC_VECTOR (7 downto 0));
38 | end DEMUX;
39 |
40 | architecture Behavioral of DEMUX is
41 | begin
42 | u1 : process (Y,A)
43 |     variable temp : std_logic_vector(0 to 7);
44 |     begin -- process u1
45 |         case A is
46 |             when "000" => temp := "0000000"&Y;
47 |             when "001" => temp := "000000"&Y&'0';
48 |             when "010" => temp := "00000"&Y&"00";
49 |             when "011" => temp := "0000"&Y&"000";
50 |             when "100" => temp := "000"&Y&"0000";
51 |             when "101" => temp := "00"&Y&"00000";
52 |             when "110" => temp := "0"&Y&"000000";
53 |             when "111" => temp := Y&"0000000";
54 |             when others => null;
55 |         end case;
56 |         D <= temp;
57 |     end process u1;
58 | end Behavioral;

```



4. Next, we need to add To add a constraint file with the".xdc" extension, as following:

```

11 | ## Switches
12 | set_property PACKAGE_PIN V17 [get_ports {Y}]
13 |     set_property IOSTANDARD LVCMOS33 [get_ports {Y}]
14 | set_property PACKAGE_PIN V16 [get_ports {A[0]}]
15 |     set_property IOSTANDARD LVCMOS33 [get_ports {A[0]}]
16 | set_property PACKAGE_PIN W16 [get_ports {A[1]}]
17 |     set_property IOSTANDARD LVCMOS33 [get_ports {A[1]}]
18 | set_property PACKAGE_PIN W17 [get_ports {A[2]}]
19 |     set_property IOSTANDARD LVCMOS33 [get_ports {A[2]}]

```

```

46  ## LEDs
47  set_property PACKAGE_PIN U16 [get_ports {D[0]}]
48      set_property IOSTANDARD LVCMOS33 [get_ports {D[0]}]
49  set_property PACKAGE_PIN E19 [get_ports {D[1]}]
50      set_property IOSTANDARD LVCMOS33 [get_ports {D[1]}]
51  set_property PACKAGE_PIN U19 [get_ports {D[2]}]
52      set_property IOSTANDARD LVCMOS33 [get_ports {D[2]}]
53  set_property PACKAGE_PIN V19 [get_ports {D[3]}]
54      set_property IOSTANDARD LVCMOS33 [get_ports {D[3]}]
55  set_property PACKAGE_PIN W18 [get_ports {D[4]}]
56      set_property IOSTANDARD LVCMOS33 [get_ports {D[4]}]
57  set_property PACKAGE_PIN U15 [get_ports {D[5]}]
58      set_property IOSTANDARD LVCMOS33 [get_ports {D[5]}]
59  set_property PACKAGE_PIN U14 [get_ports {D[6]}]
60      set_property IOSTANDARD LVCMOS33 [get_ports {D[6]}]
61  set_property PACKAGE_PIN V14 [get_ports {D[7]}]
62      set_property IOSTANDARD LVCMOS33 [get_ports {D[7]}]

```

5. Then “Run Implementation”. Select ”Number of jobs” =1 and then press OK. The implementation errors window will appear if any or the successfully completed window. From this window select “Generate Bitstream” and then OK. This will make the software generate “.bin” file to be used in programing the hardware BAYAS 3.
6. The next window will appear in which choose “Open Hardware Manger”, connect the Hardware Kit to the USB port and then press OK.From the window appears, select the “.bin” file from the Project you create by browsing for the generated “.bit file” under the “.runs” folder and program the board then press OK.
7. Complete the following truth table based on the output from your board

Data in	Selection			Data Outputs								
	Y	A2	A1	A0	D0	D1	D2	D3	D4	D5	D6	D7
0	0	0	0	0	X	X	X	X	X	X	X	X
1	0	0	0	1	X	X	X	X	X	X	X	X
0	0	0	1	X	0	X	X	X	X	X	X	X
1	0	0	1	X	1	X	X	X	X	X	X	X
0												
1												
0												
1												
0												
1												
0												
1												
0												
1												
0												
1												

Checked by \_\_\_\_\_ Date \_\_\_\_\_

## Section III. MUX and DEMUX in One Circuit

1. Repeat steps from 1 to 5 in section I
2. The Define Module Window that will appear, we will choose the input and output labels for the gates under investigation in this experiment as shown below.

Define a module and specify I/O Ports to add to your source file.  
For each port specified:  
MSB and LSB values will be ignored unless its Bus column is checked.  
Ports with blank names will not be written.

**Module Definition**

Entity name:

Architecture name:

**I/O Port Definitions**

Port Name	Direction	Bus	MSB	LSB
I	in	<input checked="" type="checkbox"/>	3	0
S	in	<input checked="" type="checkbox"/>	1	0
D	out	<input checked="" type="checkbox"/>	3	0

OK Cancel

3. In the “mux\_demux.vhd” created file, type the gates equivalent VHDL code for the 1-to-8 DEMUX between the “begin” and “end Behavioral” as follows and then save the file.

```

35     Port ( I : in STD_LOGIC_VECTOR (3 downto 0);
36           S : in STD_LOGIC_VECTOR (1 downto 0);
37           D : out STD_LOGIC_VECTOR (3 downto 0));
38 end mux_demux;
39
40 architecture Behavioral of mux_demux is
41     signal X          : STD_LOGIC;
42
43     begin
44
45     with S select
46         X <= I(0) when "00",
47             I(1) when "01",
48             I(2) when "10",
49             I(3) when "11",
50             '0'  when others;
51     u2 : process (X,S)
52         variable temp : std_logic_vector(0 to 3);
53         begin -- process u1
54             case S is
55                 when "00" => temp := "000"&X;
56                 when "01" => temp := "00"&X&'0';
57                 when "10" => temp := '0'&X&"00";
58                 when "11" => temp := X&"000";
59                 when others => null;
60             end case;
61             D <= temp;
62         end process u2;
63 end Behavioral;

```



- Next, we need to add To add a constraint file with the ".xdc" extension, as following:

```

11  ## Switches
12  set_property PACKAGE_PIN V17 [get_ports {I[0]}]
13      set_property IOSTANDARD LVCMOS33 [get_ports {I[0]}]
14  set_property PACKAGE_PIN V16 [get_ports {I[1]}]
15      set_property IOSTANDARD LVCMOS33 [get_ports {I[1]}]
16  set_property PACKAGE_PIN W16 [get_ports {I[2]}]
17      set_property IOSTANDARD LVCMOS33 [get_ports {I[2]}]
18  set_property PACKAGE_PIN W17 [get_ports {I[3]}]
19      set_property IOSTANDARD LVCMOS33 [get_ports {I[3]}]
20  set_property PACKAGE_PIN W15 [get_ports {S[0]}]
21      set_property IOSTANDARD LVCMOS33 [get_ports {S[0]}]
22  set_property PACKAGE_PIN V15 [get_ports {S[1]}]
23      set_property IOSTANDARD LVCMOS33 [get_ports {S[1]}]

```

```
60  ## LEDs
61  set_property PACKAGE_PIN U16 [get_ports {D[0]}]
62      set_property IOSTANDARD LVCMOS33 [get_ports {D[0]}]
63  set_property PACKAGE_PIN E19 [get_ports {D[1]}]
64      set_property IOSTANDARD LVCMOS33 [get_ports {D[1]}]
65  set_property PACKAGE_PIN U19 [get_ports {D[2]}]
66      set_property IOSTANDARD LVCMOS33 [get_ports {D[2]}]
67  set_property PACKAGE_PIN V19 [get_ports {D[3]}]
68      set_property IOSTANDARD LVCMOS33 [get_ports {D[3]}]
```

5. Then “Run Implementation”. Select ”Number of jobs” =1 and then press OK. The implementation errors window will appear if any or the successfully completed window. From this window select “Generate Bitstream” and then OK. This will make the software generate “.bin” file to be used in programing the hardware BAYAS 3.
6. The next window will appear in which choose “Open Hardware Manger”, connect the Hardware Kit to the USB port and then press OK. From the window appears, select the “.bin” file from the Project you create by browsing for the generated “.bit file” under the “.runs” folder and program the board then press OK.
7. List the function table (truth table) and analyze the operation.

Checked by \_\_\_\_\_ Date \_\_\_\_\_

## QUESTIONS

1. Name two applications of MUXs.

2. Given a 4-to-16 decoder with an enable line. Draw a block diagram showing how this decoder can be used as a 1-to-16 DEMUX.



3. Given two 8-to-1 MUXs with enable lines, how do you make a 16-to-1 MUX? Draw the block diagram.

4. Given a 4-to-1 MUX (M4\_1E in the symbol library), how do you obtain the Boolean function: ,

$$O = \overline{S1} S0 + S1 \overline{S0} ,$$

Show the external connection to the MUX. (Tips: Try to add the control circuits at the output, instead of inputs.)